

S. B. Roll. No.....

BASIC ELECTRICAL ENGINEERING
2nd Exam/ECE/MECHATRONIC/0961/Jun'2021
(For 2018 batch onwards)

Duration: 1.15Hrs.

M.Marks:25

SECTION-A

Q1. Attempt any three questions.

3x5=15

- i. State Kirchhoff's current and voltage laws along with suitable circuit.
- ii. State and explain Maximum power transfer theorem.
- iii. Two Resistances having resistance of 12Ω & 20Ω are connected in parallel across a 240V d.c. supply. Calculate total resistance of the circuit.
- iv. Differentiate between Magnetic and electric circuits.
- v. What is a cell? What are the differences between a primary and secondary cell?
- vi. Distinguish between A.C. and D.C.
- vii. What is power factor? Give its importance.

SECTION-B

Q2. Attempt any one question.

1x10=10

- a. Derive mathematical expression for energy stored in a magnetic field.
- b. State Norton's theorem. List the steps used for obtaining Norton's equivalent circuit.
- c. Discuss with suitable diagram the principle of operation of Wheatstone bridge and determine the condition for balance.
- d. Write a detailed note on following:-
 - i) Solar cell
 - ii) Direct voltage source