

S. B. Roll. No.....

BASIC ELECTRONICS
2nd Exam/ECE/CSE/IT/MECHATRONICS/0190/Jun'2021
(For 2018 Batch Onwards)

Duration: 1.15Hrs.

M.Marks:25

SECTION-A

Q1. Attempt any three questions.

3x5=15

- i. Explain the types of Extrinsic Semiconductor.
- ii. Classify the solids on the basis of Energy band Diagram.
- iii. Draw the circuit diagram and explain the working of Half wave rectifier
- iv. Draw and explain the VI Characteristics of Zener Diode and its applications.
- v. Explain the functions of components used in the Filter circuits.
- vi. How transistor can work as an amplifier
- vii. What do you mean by (a) Saturation region (b) Cut off (c) Active Region?

SECTION-B

Q2. Attempt any one question.

1x10=10

- a. Draw and explain the input and output characteristics of Common Base. Derive the relation between alpha and beta.
- b. What is the various method of transistor biasing? Draw and explain the circuit diagram of base resistor biasing.
- c. Define operating point of a transistor. What do you mean by stabilization of operating point?
- d. Explain the working principle of FET Amplifier. How will you determine the drain characteristics of a FET?