

S.B. Roll No.....

DIGITAL ELECTRONICS
3rd Exam/ECE/CSE/IT/0195/Jan'2022
(FOR 2018 BATCH ONWARDS)

Duration: 1.15Hrs.

M.Marks:25

SECTION-A

Q1. Attempt any three questions.

3x5=15

- a. Define shift register and explain its types.
- b. What is BCD code? What are its advantages and disadvantages?
- c. Explain and design full subtractor circuit.
- d. Give some application of Multiplexer.
- e. Give the truth table for each flip flop types: - JK, D and T.
- f. What do you mean by ripple counter?
- g. Draw the symbol, Boolean expression and truth table for EX-NOR gate.

SECTION-B

Q2. Attempt any one question.

1x10=10

- i. Draw a K-map to reduce the function. Realize the reduced function by using NAND gates only.
 $Y = \sum m (0,1,2,3,5,7,8,9,10,11,13,15).$
- ii. What is difference between asynchronous and synchronous counter.
- iii. What are D/A converter? Write the specifications of D/A converter.
- iv. What do you mean by TRI STATE buffer register? Explain the block diagram of TRI STATE buffer register