

S. B. Roll. No.....

**BASIC ELECTRONICS**  
**2<sup>nd</sup> Exam/ECE/CSE/IT/MECHATRONIC/0190/Jun'2022**  
**(For 2018 Batch Onwards)**

**Duration: 3Hrs.**

**M.Marks:75**

**SECTION-A**

**Q1. Give answer in one line.**

**15x1=15**

- a. What are majority carriers in n-type semiconductors
- b. Pure semiconductor is doped with what kind of impurity (name with valency) to get p-type semiconductor.
- c. What is the value of barrier potential in Silicon
- d. What happens to the depletion layer when we reverse bias a diode?
- e. No. Of diodes used in half wave, full wave centre tap and bridge rectifier
- f. Give relation between  $\alpha$  and  $\beta$
- g. Name the three layers of transistor.
- h. Out of the three layers of transistor, which one is heavily doped?
- i. Name the junction in a transistor which is forward biased for proper working.
- j. What is the phase difference between input and output waveform in common emitter amplifier
- k. Name a device (diode) which shows negative resistance
- l. Draw symbol of a pnp transistor
- m. Which diode is used as a voltage regulator
- n. Name the three terminals of JFET
- o. What is full form of PIV

**SECTION-B**

**Q2. Attempt any six questions.**

**6x5=30**

- i. Classify different type of semiconductors.
- ii. Explain the concept of depletion layer. Why it is so called?
- iii. Draw and explain the characteristics of p-n junction diode.
- iv. Explain concept of rectifier efficiency and ripple factor.
- v. Explain the working of a transistor in common base mode.
- vi. Derive relation between  $\alpha$  and  $\gamma$ .
- vii. Give three reasons why biasing is essential.
- viii. Explain voltage divider biasing.
- ix. Explain with diagram the operation of enhancement type MOSFET.

**SECTION-C**

**Q3. Attempt any three questions.**

**3x10=30**

- a. Explain with wave-shapes the full wave Bridge rectifier circuit.
- b. Draw and explain single stage transistor amplifier circuit
- c. Compare JFET, MOSFET, BJT
- d. Draw and explain the input and output characteristics of common emitter configuration of transistor.
- e. Explain the construction and working of JFET