

S. B. Roll. No.....

NETWORK FILTERS AND TRANSMISSION LINES
4th Exam/ECE/3061/Jun'2022
(For 2018 Batch Onwards)

Duration: 3Hrs.

M.Marks:75

SECTION-A

Q1. Give answer in one line.

15x1=15

- a. Give full form of VSWR.
- b. Define 2-port network.
- c. Attenuation is the term that is exactly reverses of?
- d. Name the primary constants of Transmission line.
- e. Write full form of LPF.
- f. Define Active network.
- g. Write the condition for a line to become distortionless.
- h. Write any one limitation of passive filters.
- i. Name any two major losses in Transmission line.
- j. Write the units of attenuation.
- k. Name any one commonly used type of active filter.
- l. In Crystal filters, which effect is used?
- m. Write any one application of Transmission line.
- n. Give one example of bilateral element.
- o. Define Ladder network.

SECTION-B

Q2. Attempt any six questions.

6x5=30

- i. Describe Insertion loss in 2-port network.
- ii. What are the disadvantages of Constant-K filters?
- iii. Derive the relation between decibel and neper.
- iv. Differentiate between Band pass filter and Band stop filter.
- v. Explain the concept of Characteristic impedance.
- vi. What is reflection in Transmission lines?
- vii. Define attenuator and write its uses.
- viii. What is meant by Line loading? Why is it done?

SECTION-C

Q3. Attempt any three questions.

3x10=30

- a. Explain the concept of impedance matching using Single Stub.
- b. Define Filter. Give its classification and uses.
- c. Explain the properties of asymmetrical network.
- d. Explain different types of Transmission line.
- e. Write a short note (**any two**) i) Standing wave ratio ii) m-derived filter iii) High pass filter