

S. B. Roll. No.....

**BASIC ELECTRONICS**  
**2<sup>nd</sup> Exam/ECE/IT/CSc/Mechatronic/0190/Dec'22**  
**(For 2018 Batch Onwards)**

**Duration: 3Hrs.**

**M.Marks:75**

**SECTION-A**

**Q1. Do as directed.**

**15x1=15**

- a. Valence electrons are present in which orbit of an atom?
- b. The majority carriers in N-type semiconductor are \_\_\_\_\_.
- c. How many diodes are used in Bridge rectifier?
- d. The ripple factor of Half wave rectifier is \_\_\_\_\_.
- e. The rectifier efficiency of Half- wave rectifier is \_\_\_\_\_.
- f. Draw circuit symbol of Zener diode.
- g. Name different terminals of a transistor.
- h. In any transistor circuit,  $I_E = \text{_____} + \text{_____}$
- i. Draw circuit symbol of NPN transistor.
- j. In transistor base is made very \_\_\_\_\_ and it is \_\_\_\_\_ doped.
- k. The ideal value of stability factor is \_\_\_\_\_.
- l. The d. c. load line is a plot of \_\_\_\_\_ and \_\_\_\_\_.
- m. The output impedance of a transistor amplifier in CB mode is very \_\_\_\_\_.
- n. MOSFET has \_\_\_\_\_ Terminals.
- o. The input impedance of an FET is \_\_\_\_\_ than that of BJT.

**SECTION-B**

**Q2. Attempt any six questions.**

**6x5=30**

- i. Write a note on P-type semiconductor.
- ii. Explain doping briefly?
- iii. Write a short note on Zener diode.
- iv. Explain the working of PNP transistor with diagram.
- v. Why CE configuration is commonly used?
- vi. Define transistor biasing.
- vii. Compare JFET with Ordinary transistor.
- viii. What is ripple factor? How it can be minimized?

**SECTION-C**

**Q3. Attempt any three questions.**

**3x10=30**

- a. Discuss the Half wave rectifier with diagram.
- b. Discuss the working of filter circuits used in rectifiers.
- c. Draw and explain the characteristics of common emitter configuration.
- d. Explain potential divider bias circuit in detail.
- e. Explain the construction and working of FET.