

S. B. Roll. No.....

ELECTRONICS DEVICES AND CIRCUITS
3rd Exam/ECE/5861/Dec'22
(For 2018 Batch Onwards)

Duration: 3Hrs.

M.Marks:75

SECTION-A

Q1. Fill in the blanks.

15x1=15

- a. Positive feedback is used in _____.
- b. An op-amp has _____ number of inputs.
- c. Push-pull amplifier uses _____ transistors.
- d. An astable multi vibrator generates _____ waves
- e. CMRR stands for _____
- f. Maximum efficiency of Class-B amplifier is _____.
- g. In multi-stage voltage amplifier _____ coupling is used,
- h. IC 555 is a _____ circuit.
- i. To cool down power transistors _____ are used.
- j. The output voltage of a 7412 IC voltage regulator is _____ volts.
- k. Input impedance of ideal op-amp is _____
- l. Amplifier amplifies _____ signal.
- m. Very small frequency signals are amplified by using _____ coupling.
- n. The resistance of a loudspeaker is usually _____.
- o. At resonance a parallel tuned circuit offers _____ impedance.

SECTION-B

Q2. Attempt any six questions.

6x5=30

- i. What is the need of Multi-stage Amplifier?
- ii. Give the advantages of negative feedback.
- iii. Compare Voltage and Power amplifiers.
- iv. Explain Class-A amplifier.
- v. Explain parallel resonant circuit.
- vi. What are different types of wave-shaping circuits?
- vii. What is a regulated DC power supply?

SECTION-C

Q3. Attempt any three questions.

3x10=30

- a. Explain the principle and working of Wein's-bridge oscillator
- b. Draw the block diagram of IC 555 and give its working.
- c. Describe RC coupled amplifier and its working with advantages and disadvantages.
- d. How op-amp is used as an adder?
- e. Give a comparison of Class A, Class B, Class C and Class AB amplifiers.